

CS224_2021_quiz1_A

...

Points: 14/20

1. Write Verilog code to design a 8-bit Barrel shifter that rotates the input number 'a' by an arbitrary number of positions to the right. The number of positions to rotate is given as a control input 'ctrl' which is a 3-bit value. Use 'case' statement to design the module. The output will go in variable 'out'.

Write the Verilog code for this with help of Xilinx ISE and paste it in the space below.

(2/8 Points)

```
module barrel(
    input [7:0] A,
    input [2:0] ctrl,
    output reg [7:0] out
);

always@(*)
    begin
        case(ctrl)
            3'b000 : begin
                out[0]= A[0];
                out[1]= A[1];
                out[2]= A[2];
                out[3]= A[3];
                out[4]= A[4];
                out[5]= A[5];
                out[6]= A[6];
                out[7]= A[7];
            end

            3'b001 : begin
                out[0]= A[7];
                out[1]= A[0];
                out[2]= A[1];
                out[3]= A[2];
                out[4]= A[3];
                out[5]= A[4];
                out[6]= A[5];
                out[7]= A[6];
            end

            3'b010 : begin
                out[0]= A[6];
                out[1]= A[7];
                out[2]= A[0];
                out[3]= A[1];
                out[4]= A[2];
                out[5]= A[3];
                out[6]= A[4];
                out[7]= A[5];
            end

            3'b011 : begin
                out[0]= A[5];
                out[1]= A[6];
                out[2]= A[7];
                out[3]= A[0];
                out[4]= A[1];
                out[5]= A[2];
                out[6]= A[3];
                out[7]= A[4];
            end
        endcase
    end
endmodule
```

```

                                end
3'b100 : begin
                                out[0]= A[4];
                                out[1]= A[5];
                                out[2]= A[6];
                                out[3]= A[7];
                                out[4]= A[0];
                                out[5]= A[1];
                                out[6]= A[2];
                                out[7]= A[3];
                                end

3'b101 : begin

                                out[0]= A[3];
                                out[1]= A[4];
                                out[2]= A[5];
                                out[3]= A[6];
                                out[4]= A[7];
                                out[5]= A[0];
                                out[6]= A[1];
                                out[7]= A[2];
                                end

3'b110 : begin
                                out[0]= A[2];
                                out[1]= A[3];
                                out[2]= A[4];
                                out[3]= A[5];
                                out[4]= A[6];
                                out[5]= A[7];
                                out[6]= A[0];
                                out[7]= A[1];
                                end

3'b111 : begin
                                out[0]= A[1];
                                out[1]= A[2];
                                out[2]= A[3];
                                out[3]= A[4];
                                out[4]= A[5];
                                out[5]= A[6];
                                out[6]= A[7];
                                out[7]= A[0];
                                end

                                endcase
                                end

endmodule
```

□ "you have done rotate left"

2. For the barrel shifter designed in previous question, write the components synthesised in the RTL. Use the synthesis report to write this answer.
(2/2 Points)

one 8-bit 8-to-1 multiplexer

3. Modify the barrel shifter code from previous question and design a 4-bit barrel shifter. This 4-bit shifter has one more input 'dir' which indicates the direction of rotation. if dir=1 rotate right else rotate left. Write the Verilog code for this with help of Xilinx ISE and paste it in the space below.
(8/8 Points)

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 14:30:48 02/02/2021
// Design Name:
// Module Name: barrel4
// Project Name:
// Target Devices:
// Tool versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module barrel4(
    input [3:0] A,
    input dir,
    input [1:0] ctrl,
    output reg [3:0] out
);
always@(*)
    begin
        case(ctrl)
            3'b000 : begin
                case(dir)
                    1'b0:begin

                        out[0]= A[0];
                        out[1]= A[1];
                        out[2]= A[2];
                        out[3]= A[3];
                        end
                    1'b1:begin

                        out[0]= A[0];
                        out[1]= A[1];
                        out[2]= A[2];
                        out[3]= A[3];
                        end
                endcase
            endcase
        end

            3'b001 : begin
                case(dir)
                    1'b0:begin

```

```
    out[0]= A[1];  
    out[1]= A[2];  
    out[2]= A[3];  
    out[3]= A[0];  
    end  
    1'b1:begin
```

```
    out[0]= A[3];  
    out[1]= A[0];  
    out[2]= A[1];  
    out[3]= A[2];  
    end  
endcase  
end
```

```
3'b010 : begin  
case(dir)
```

```
    1'b0:begin
```

```
    out[0]= A[2];  
    out[1]= A[3];  
    out[2]= A[0];  
    out[3]= A[1];  
    end  
    1'b1:begin
```

```
    out[0]= A[2];  
    out[1]= A[3];  
    out[2]= A[0];  
    out[3]= A[1];  
    end  
endcase  
end
```

```
3'b011 : begin  
case(dir)
```

```
    1'b0:begin
```

```
    out[0]= A[3];  
    out[1]= A[0];  
    out[2]= A[1];  
    out[3]= A[2];  
    end  
    1'b1:begin
```

```
    out[0]= A[1];  
    out[1]= A[2];  
    out[2]= A[3];  
    out[3]= A[0];  
    end  
endcase  
end
```

```
        endcase
    end

endmodule
```

4. For the new barrel shifter in Q-3 write the components synthesised in the RTL.
Use the synthesis report to write this answer
(2/2 Points)

4-bit 2-to-1 multiplexer	: 2
4-bit 4-to-1 multiplexer	: 1

This content is created by the owner of the form. The data you submit will be sent to the form owner. Microsoft is not responsible for the privacy or security practices of its customers, including those of this form owner. Never give out your password.

Powered by Microsoft Forms | [Privacy and cookies](#) | [Terms of use](#)