 


CS224_2021_quiz3_A

...

Points: 15/20

1



For the FSM given in the figure, write the Verilog code. Put your answers from Q-2 onward as this question is not graded.

Use 'x' as input variable and 'y' as output variable.

The other inputs are 'clk' and 'reset' 

declarations in q2

2

Write the Verilog code statements to change the current state. Use 'x' as input variable and 'y' as output variable.

(2/2 Points)

```
//Includes declarations
module q1(
    input x,
    input reset,
    input clk,
    output reg y
);
reg[2:0] curr, nex;
parameter a = 3'b000;
parameter b = 3'b001;
parameter c = 3'b010;
parameter d = 3'b011;
parameter e = 3'b100;

always@(posedge clk or posedge reset)
begin
    if(reset) curr = 0;
    else curr = nex;
end
```

3

Write Verilog code statements for next state and output logic

(10/10 Points)

```

// See q2 for declarations
always@(x or curr)
begin
    case(curr)
    a :
    begin
        if(x == 0) begin nex = a; #2 y = 0; end
        else begin nex = b; #2 y = 0; end
    end
    b :
    begin
        if(x == 0) begin nex = c; #2 y = 0; end
        else begin nex = d; #2 y = 0; end
    end
    c :
    begin
        if(x == 0) begin nex = a; #2 y = 0; end
        else begin nex = d; #2 y = 0; end
    end
    d :
    begin
        if(x == 0) begin nex = e; #2 y = 0; end
        else begin nex = d; #2 y = 1; end
    end
    e :
    begin
        if(x == 0) begin nex = a; #2 y = 0; end
        else begin nex = d; #2 y = 1; end
    end
    default : nex = a;
    endcase
end

```

For the testbench code given below, paste that in your testbench file and generate the output. Paste the output of the monitor after running the testbench in the space below.

```
initial begin
clk = 0; forever clk = #5 ~clk;
end
```

```
initial begin
$monitor($time, " x=%b, y=%b ", x, y);
reset = 1; x=0;
#10; reset = 0;
#10; x = 0;
#12; x = 1; #5; x=0;
#17; x = 1; #3; x=0;
#17; x = 1; #18; x = 0;
#12; x = 1; #5; x=0;
end
```

(3/8 Points)

```
0 x=0, y=x
  2 x=0, y=0
 32 x=1, y=0
 37 x=0, y=0
 54 x=1, y=0
 57 x=0, y=0
 74 x=1, y=0
 76 x=1, y=1
 92 x=0, y=1
 94 x=0, y=0
104 x=1, y=0
106 x=1, y=1
109 x=0, y=1
111 x=0, y=0
```

