

CS224_2021_quiz1_B

...

Points: 30/20


1

For the circuit diagram given below, write structural Verilog code. Write separate modules for the required basic gates. Full adder is also a separate module, you can write behavioural code for it.

Use these modules to build your complete design.

Add a constant delay of 2 units in the basic gate and 2 units for both sum and carry-out in full-adder.

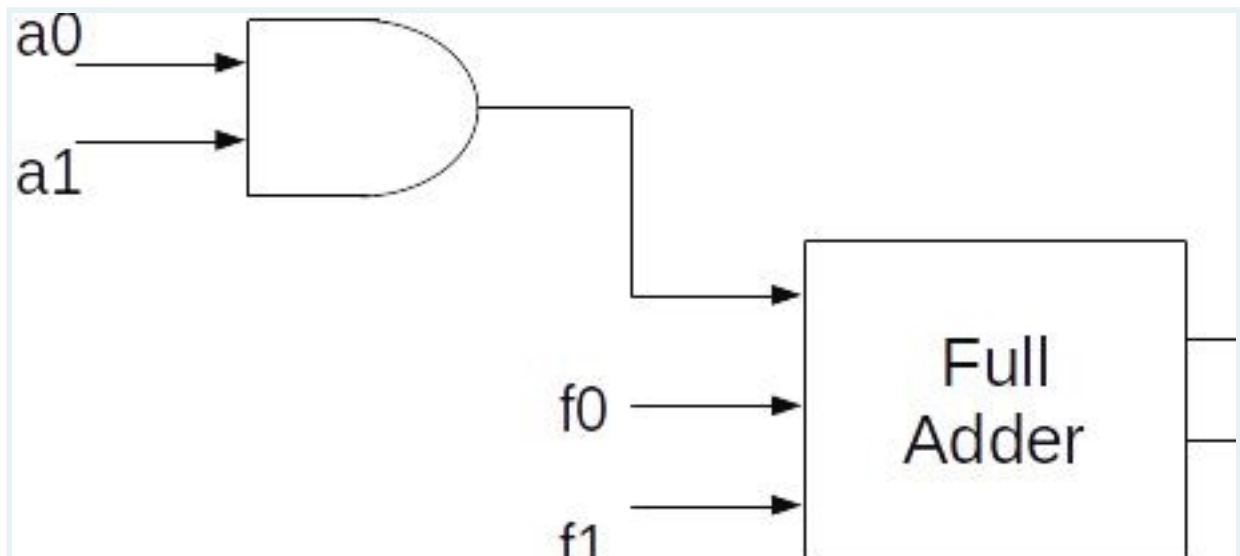Synthesise the design and check if RTL matches the given diagram. 



Yes RTL Matches

2

Write the code of basic gate.
(2/2 Points)

```
module andgate(  
    input a0,  
    input a1,  
    output out  
);  
assign #2 out = a0&a1;  
  
endmodule
```

3

Write the code for full adder.
(4/4 Points)

```
module full_adder(  
    input a0,  
    input a1,  
    input a2,  
    output sum,  
    output car  
);  
  
assign #2 sum = a0^a1^a2;  
assign #2 car = a0&a1 | a1&a2 | a2&a0;  
endmodule
```

4

Write the code for the circuit diagram showing instantiations of modules
(4/4 Points)

```
module final(  
    input a0,  
    input a1,  
    input f0,  
    input f1,  
    output sum,  
    output cout  
);  
wire g;  
andgate and1(a0, a1, g);  
full_adder fa1(g, f0, f1, sum, cout);  
  
endmodule
```

5

Write test-bench for the design to identify the delay taken by the circuit to give the final output sum and carry-out. It should demonstrate the output coming after 2 and 4 time units. Use monitor commands to print the output.

Give appropriate test cases and paste the test-bench code below.

Your test-bench will have all signals 0 at time=0.

At time=10ns change the inputs to new values.

(2/2 Points)

```

module final_test_bench;

    // Inputs
    reg a0;
    reg a1;
    reg f0;
    reg f1;

    // Outputs
    wire sum;
    wire cout;

    // Instantiate the Unit Under Test (UUT)
    final uut (
        .a0(a0),
        .a1(a1),
        .f0(f0),
        .f1(f1),
        .sum(sum),
        .cout(cout)
    );
    always@*
        $monitor("time : ", $time , " a0 = %b , a1 = %b, f0 = %b , f1 = %b , sum = %b, cout = %b "
,a0, a1, f0, f1, sum, cout) ;

    initial begin
        // Initialize Inputs
        a0 = 0;
        a1 = 0;
        f0 = 0;
        f1 = 0;
        //2 unit delay
        #10;
        a0 = 0;
        a1 = 1;
        f0 = 0;
        f1 = 1;

        //4 unit delay
        #10;
        a0 = 1;
        a1 = 1;
        f0 = 0;
        f1 = 1;

    end

endmodule

```

6

Generate the waveform and output of monitor.

Paste the output of monitor command showing delay of 2 units to generate final output.

(4/4 Points)

```
time :      0 a0 = 0 , a1 = 0, f0 = 0 , f1 = 0 , sum = x, cout = x
time :      2 a0 = 0 , a1 = 0, f0 = 0 , f1 = 0 , sum = x, cout = 0
time :      4 a0 = 0 , a1 = 0, f0 = 0 , f1 = 0 , sum = 0, cout = 0
time :     10 a0 = 0 , a1 = 1, f0 = 0 , f1 = 1 , sum = 0, cout = 0
time :     12 a0 = 0 , a1 = 1, f0 = 0 , f1 = 1 , sum = 1, cout = 0
time :     20 a0 = 1 , a1 = 1, f0 = 0 , f1 = 1 , sum = 1, cout = 0
time :     24 a0 = 1 , a1 = 1, f0 = 0 , f1 = 1 , sum = 0, cout = 1
```

lines 4 and 5 show a 2s delay

7

Generate the waveform and output of monitor.

Paste the output of monitor command showing delay of 4 units to generate final output.

(4/4 Points)

```
time :      0 a0 = 0 , a1 = 0, f0 = 0 , f1 = 0 , sum = x, cout = x
time :      2 a0 = 0 , a1 = 0, f0 = 0 , f1 = 0 , sum = x, cout = 0
time :      4 a0 = 0 , a1 = 0, f0 = 0 , f1 = 0 , sum = 0, cout = 0
time :     10 a0 = 0 , a1 = 1, f0 = 0 , f1 = 1 , sum = 0, cout = 0
time :     12 a0 = 0 , a1 = 1, f0 = 0 , f1 = 1 , sum = 1, cout = 0
time :     20 a0 = 1 , a1 = 1, f0 = 0 , f1 = 1 , sum = 1, cout = 0
time :     24 a0 = 1 , a1 = 1, f0 = 0 , f1 = 1 , sum = 0, cout = 1
```

LAST 2 lines show a 4s delay

This content is created by the owner of the form. The data you submit will be sent to the form owner. Microsoft is not responsible for the privacy or security practices of its customers, including those of this form owner. Never give out your password.

Powered by Microsoft Forms | [Privacy and cookies](#) | [Terms of use](#)